


EE635

Digital IC Design

Course Project Report

Group 8 - Jatin, Harshith, Mehak, Ruthwik



Basic Theory of Full Adder :

 


$$\text{Sum } s = a \oplus b \oplus c_i$$

$$\text{carry } c_o = ab + bc_i + c_i a$$

4-Bit Adder as discussed in class :

  


Sum implementation

 


c_o implementation

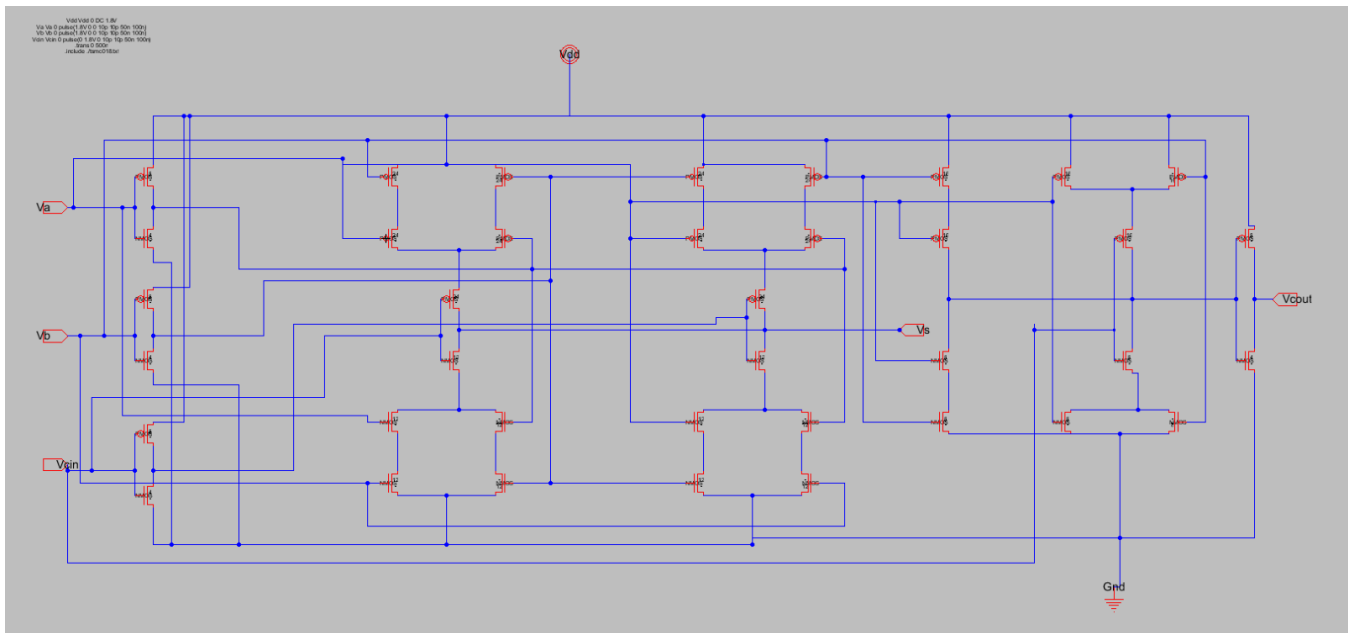Un-Optimised Full Adder Schematic (As discussed in class) :




Propagation Delays of Un-Optimised Full Adder :

 Case 1 : A,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)




tpHL = 423.08 ps

 


tpLH = 559.17 ps

 Case 2 : A = 0 \rightarrow 1 (Low to High) ,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)




tpHL = 443.66 ps

 


tpLH = 528.57 ps

 Case 3 : A = 0 \rightarrow 1 (Low to High) ,B = 1 \rightarrow 0 (High to Low), Cin = 1 \rightarrow 0 (High to Low)



tpHL = 433.92 ps

 

tpLH = 402.23 ps

Overall Propagation Delays in Tabulated Form for the Un-Optimised Full Adder :

	tpHL	tpLH	tp = (tpHL + tpLH) / 2
A,B = 1 → 0, C = 0 → 1	423.08 ps	559.17 ps	491.12 ps
A,C = 0 → 1, B = 1 → 0	443.66 ps	528.57 ps	486.115 ps
A = 0 → 1, B, C = 1 → 0	433.92 ps	402.23 ps	418.07 ps

Optimisation Idea and Technique :

Optimisation Idea and Technique :

a	b	c _i	s	c _o
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \sum m(1, 2, 5, 7)$$

$$\bar{S} = \sum m(0, 3, 4, 6)$$

$$C_o = \sum m(3, 5, 6, 7)$$

$$\bar{C}_o = \sum m(0, 1, 2, 4)$$

\therefore S and C_o can be implemented using minnion logic


$$C_{out} = AB + BC_{in} + C_{in}A$$

$$S = A \oplus B \oplus C_{in}$$

$$= A(\overline{B \oplus C_{in}}) + \overline{A} (B \oplus C_{in})$$


$$= A(\overline{BC_{in}} + \overline{B} \overline{C_{in}}) + \overline{A} (BC_{in} + \overline{B} \overline{C_{in}})$$
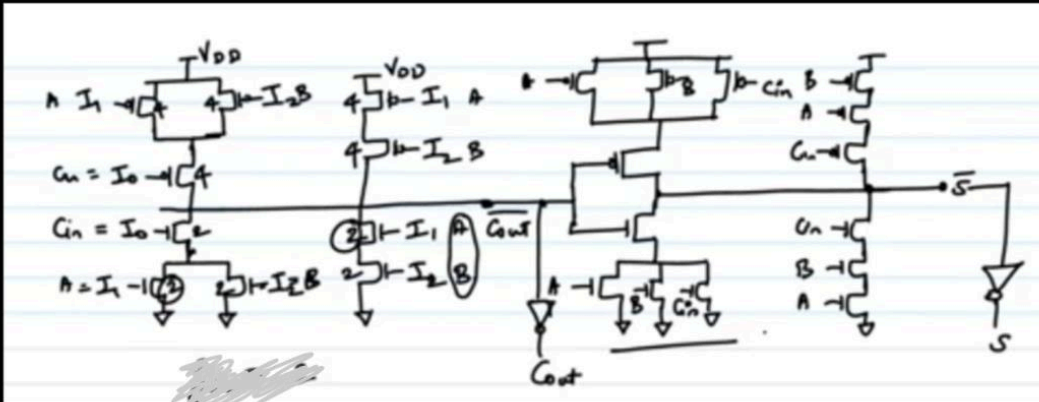
$$\therefore S = ABC_{in} + \overline{C}_o (A + B + C_{in})$$




Q2. A) Optimize the full adder given in 1(a) using more efficient topologies than what is discussed in the class. Construct the VTC and find out the propagation delays (both pre- and post-layout levels) of the circuit assuming that all inputs transition simultaneously.

Optimised Full Adder Schematic :

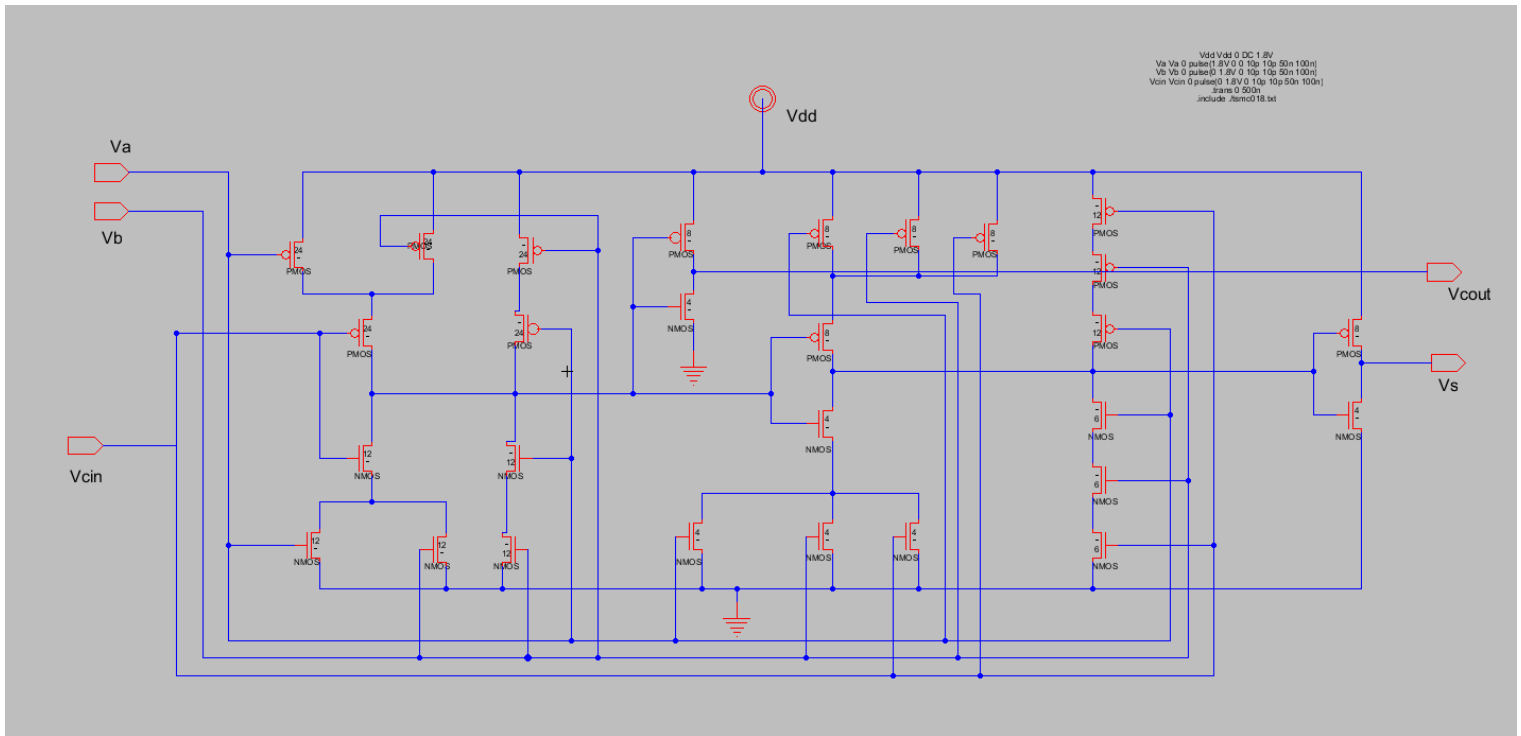


Output Waveforms of Optimised Full Adder using Schematic Simulations :


Case 1 : A,B = 1 → 0 (High to Low), Cin = 0 → 1 (Low to high)

 

Case 2 : A = 0 → 1 (Low to High) ,B = 1 → 0 (High to Low), Cin = 0 → 1 (Low to high)

 


 Case 3 : A = 0 \rightarrow 1 (Low to High) ,B = 1 \rightarrow 0 (High to Low), Cin = 1 \rightarrow 0 (High to Low)




VTC of Optimised Full Adder using Schematic Simulations :

Case 1 : A,B,Cin = 1 \rightarrow 0 (High to Low)

 

 Case 2 : A,B, = 0 \rightarrow 1 (Low to High)



Propagation Delays of Optimised Full Adder using Schematic Simulations :

Case 1 : A,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)

```
Warning: Ps = 0 is less than W.  
Direct Newton iteration for .op point succeeded.  
  
prop_delay1=-4.85107e-009 FROM 5.0015e-009 TO 1.50432e-010  
prop_delay2=6.58562e-011 FROM 5.0015e-009 TO 5.06736e-009  
  
Date: Thu Apr 24 17:12:16 2025  
Total elapsed time: 0.349 seconds.  
  
tnom = 27  
temp = 27  
method = modified trap  
totiter = 7173  
traniter = 7123  
tranpoints = 2256  
accept = 1936  
rejected = 320  
matrix size = 22  
fillins = 0
```

Propagation Delay : 65.85 ps

Case 2 : A = 0 \rightarrow 1 (Low to High) ,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)

```
Warning: Ps = 0 is less than W.  
Direct Newton iteration for .op point succeeded.  
  
prop_delay1=5.11322e-009 FROM 5e-013 TO 5.11372e-009  
prop_delay2=4.39523e-011 FROM 5e-013 TO 4.44523e-011  
  
Date: Thu Apr 24 17:18:30 2025  
Total elapsed time: 0.403 seconds.  
  
tnom = 27  
temp = 27  
method = modified trap  
totiter = 7112  
traniter = 7081  
tranpoints = 2336  
accept = 2013  
rejected = 323  
matrix size = 22  
fillins = 0  
solver = Normal  
Matrix Compiler1: 1.61 KB object code size 0.4/0.3/10.31
```

Propagation Delay : 43.95 ps

Case 3 : $A = 0 \rightarrow 1$ (Low to High) , $B = 1 \rightarrow 0$ (High to Low), $C_{in} = 1 \rightarrow 0$ (High to Low)

```
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.

prop_delay1=4.48429e-011 FROM 5e-013 TO 4.53429e-011
prop_delay2=3.23986e-011 FROM 5e-013 TO 3.28986e-011


Date: Thu Apr 24 17:20:07 2025
Total elapsed time: 0.330 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 7087
traniter = 7063
tranpoints = 2280
accept = 1988
rejected = 292
matrix size = 22
fillins = 0
solver = Normal
Thread vector: 19.5/11.5[2] 2.1/2.0[1] 0.8/0.9[1] 0.1/0.7[1] 2592/500
Matrix Compiler1: 1.61 KB object code size 0.3/0.1/[0.1]
```

Propagation Delay : 32.39 ps

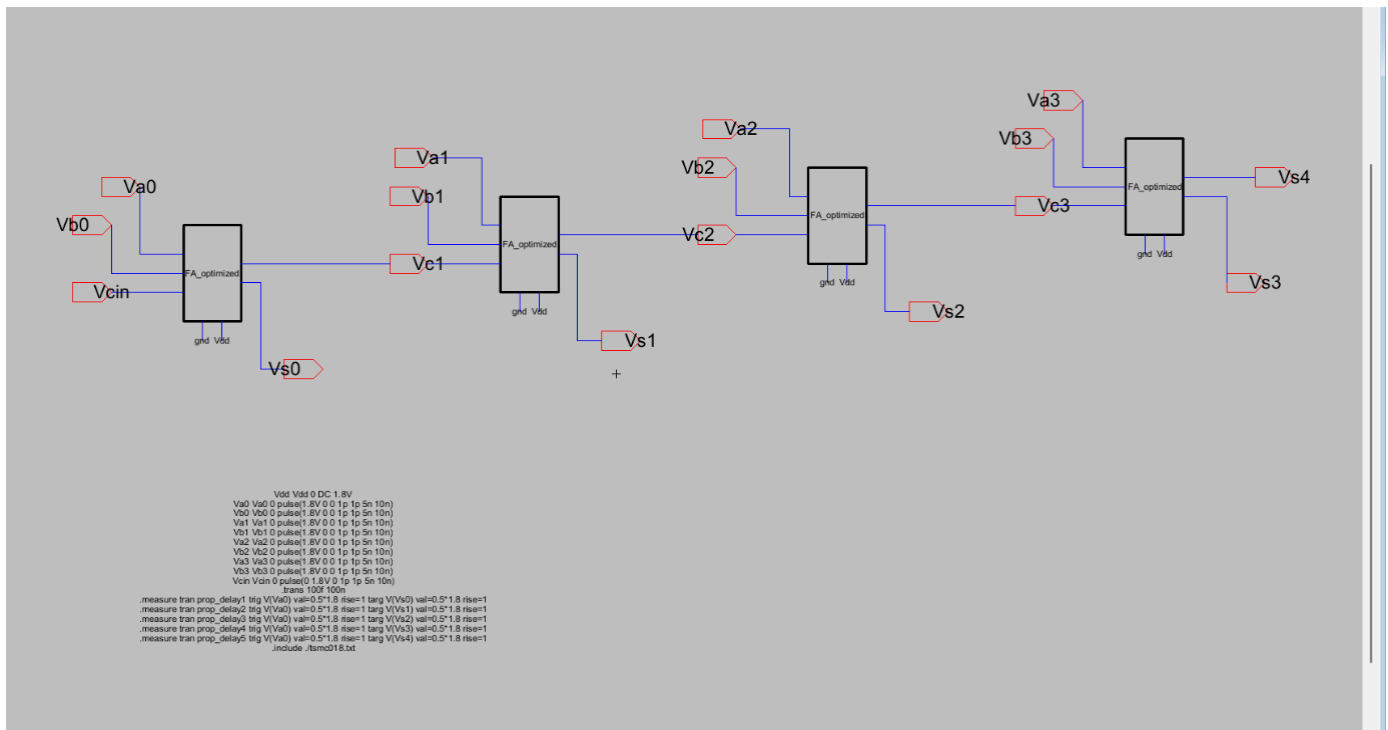
Q2.B) Build an optimized 4-bit adder using the full adder above with or without using additional logic. Demonstrate the functionality through waveforms for 2-3 different input combinations. Estimate the critical path delay through simulations.

Optimised Four-Bit Adder Schematic (by repeating optimised Full Adder Blocks) :




Output Graphs of Optimised Four-Bit Adder using Schematic Simulations :



Case 1 : $a_0, a_1, a_2, a_3 = 1 \rightarrow 0$; $b_0, b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$

 

Case 2 : $a_0, a_1, a_2 = 0 \rightarrow 1$; $b_0, a_3 = 1 \rightarrow 0$; $b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 1 \rightarrow 0$

 

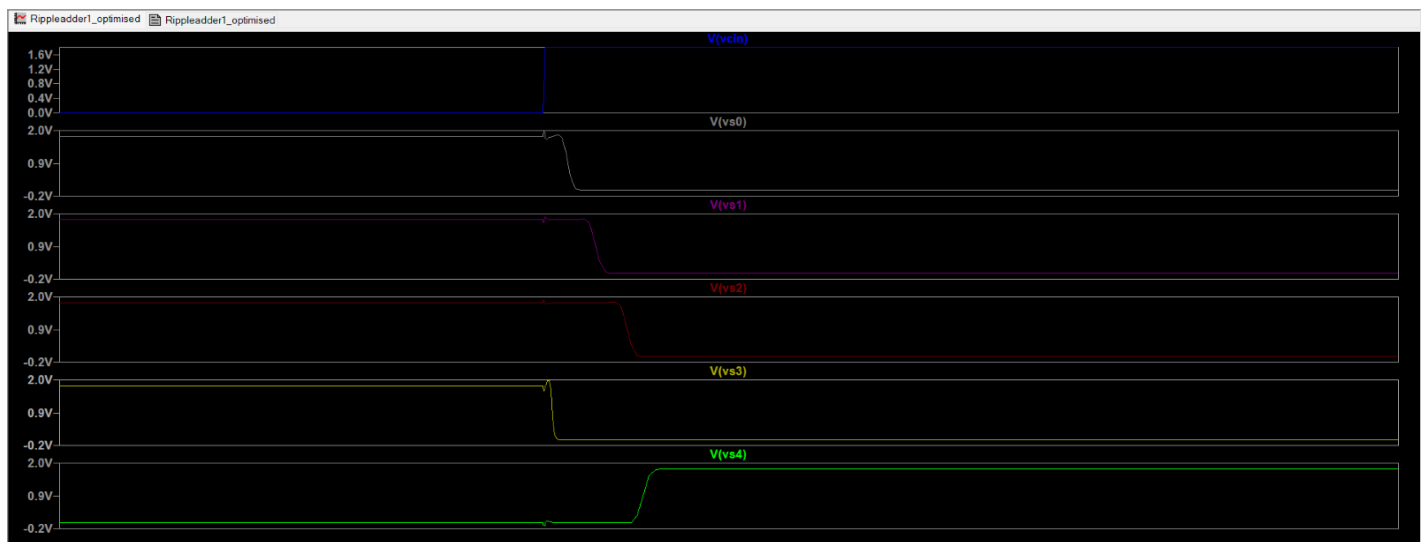 Case 3 : $a_0, a_2, b_1 = 0 \rightarrow 1$; $a_1, b_0, a_3, b_3, b_2 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$



Critical Path Delays for Optimised Four-Bit Adder : (We use S3 for critical path delay)

Case 1 : $a_0, a_1, a_2, a_3 = 1 \rightarrow 0$; $b_0, b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$

```
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.

prop_delay1=-4.85881e-009 FROM 5.0015e-009 TO 1.42692e-010
prop_delay2=2.26357e-010 FROM 5.0015e-009 TO 5.22786e-009
prop_delay3=2.2773e-010 FROM 5.0015e-009 TO 5.22923e-009
prop_delay4=2.27621e-010 FROM 5.0015e-009 TO 5.22912e-009
prop_delay5=6.34556e-011 FROM 5.0015e-009 TO 5.06496e-009

Date: Thu Apr 24 17:02:03 2025
Total elapsed time: 0.992 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 8127
traniter = 8077
```

Propagation Delay : 227.62 ps

Case 2 : $a_0, a_1, a_2 = 0 \rightarrow 1$; $b_0, a_3 = 1 \rightarrow 0$; $b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 1 \rightarrow 0$

```
SPICE Error Log: C:\EE635\4FA_optimized.log
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.


prop_delay1=1.18229e-010 FROM 5e-013 TO 1.18729e-010
prop_delay2=2.78668e-010 FROM 5e-013 TO 2.79168e-010
prop_delay3=5.34747e-009 FROM 5e-013 TO 5.34797e-009
prop_delay4=2.9181e-010 FROM 5e-013 TO 2.9231e-010
prop_delay5=5.21636e-009 FROM 5e-013 TO 5.21686e-009

Date: Thu Apr 24 17:46:36 2025
Total elapsed time: 1.368 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 8396
```

Propagation Delay : 291.81 ps

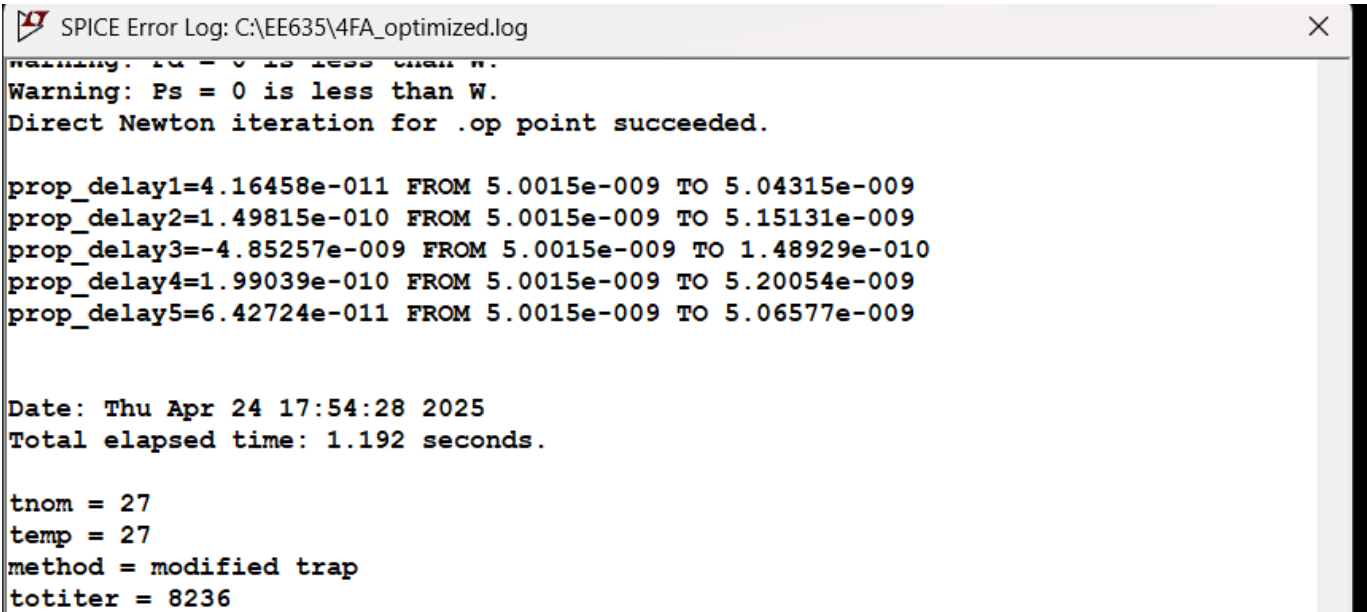Case 3 : $a_0, a_2, b_1 = 0 \rightarrow 1$; $a_1, b_0, a_3, b_3, b_2 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$



SPICE Error Log: C:\EE635\4FA_optimized.log

Warning: $P_s = 0$ is less than W .
Warning: $P_s = 0$ is less than W .
Direct Newton iteration for .op point succeeded.

prop_delay1=4.16458e-011 FROM 5.0015e-009 TO 5.04315e-009
prop_delay2=1.49815e-010 FROM 5.0015e-009 TO 5.15131e-009
prop_delay3=-4.85257e-009 FROM 5.0015e-009 TO 1.48929e-010
prop_delay4=1.99039e-010 FROM 5.0015e-009 TO 5.20054e-009
prop_delay5=6.42724e-011 FROM 5.0015e-009 TO 5.06577e-009


Date: Thu Apr 24 17:54:28 2025
Total elapsed time: 1.192 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 8236

Propagation Delay : 199.03 ps


Post-Layout Simulations :

Optimised Full Adder Layout :

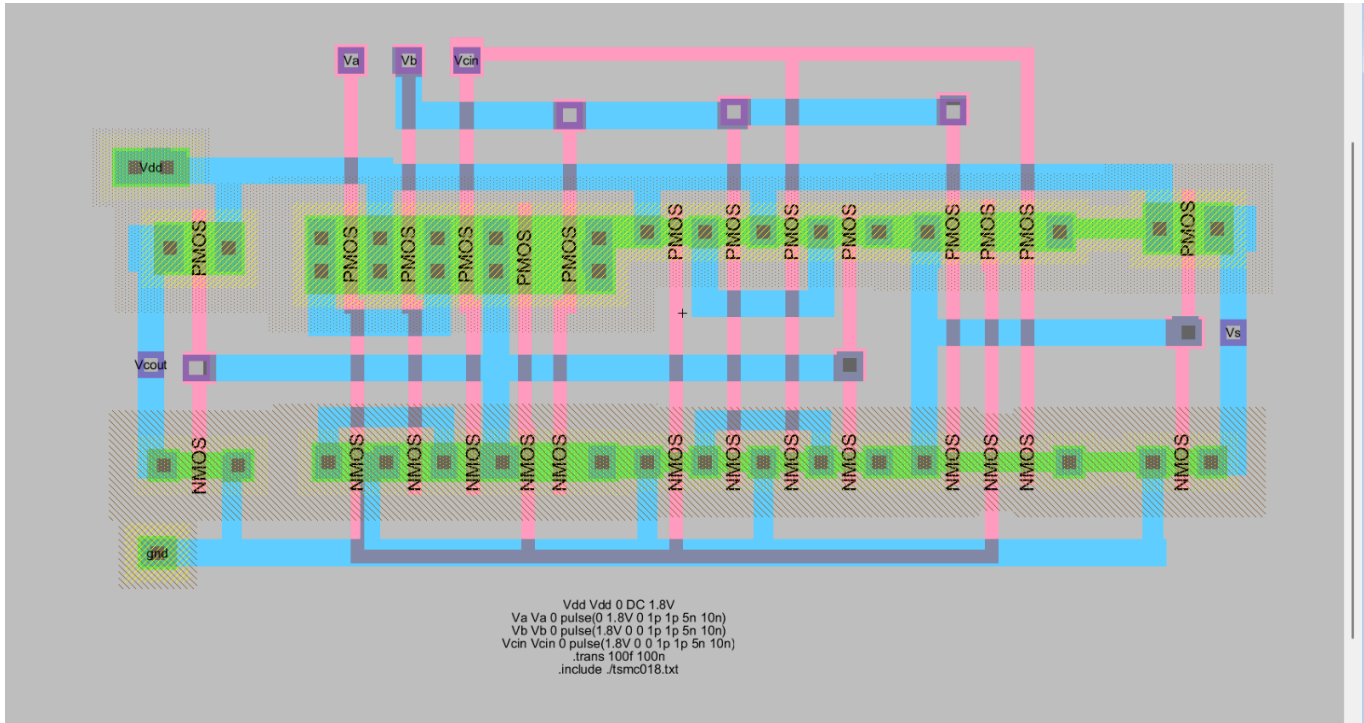


Output Waveforms of Optimised Full Adder using Schematic Simulations :


Case 1 : A,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)

 

Case 2 : A = 0 \rightarrow 1 (Low to High) ,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)

 


 Case 3 : $A = 0 \rightarrow 1$ (Low to High) , $B = 1 \rightarrow 0$ (High to Low), $C_{in} = 1 \rightarrow 0$ (High to Low) :




VTC of Optimised Full Adder using Layout Simulations :


Case 1: $A = B = 0 \rightarrow 1$, $C_{in} = 1$

 

Case 2: $A = B = 1 \rightarrow 0$, $C_{in} = 0$

 


Case 3: A = B = Cin = 1 → 0

 

Propagation Delays of Optimised Full Adder using Layout Simulations :


Case 1 : A,B = 1 \rightarrow 0 (High to Low), Cin = 0 \rightarrow 1 (Low to high)

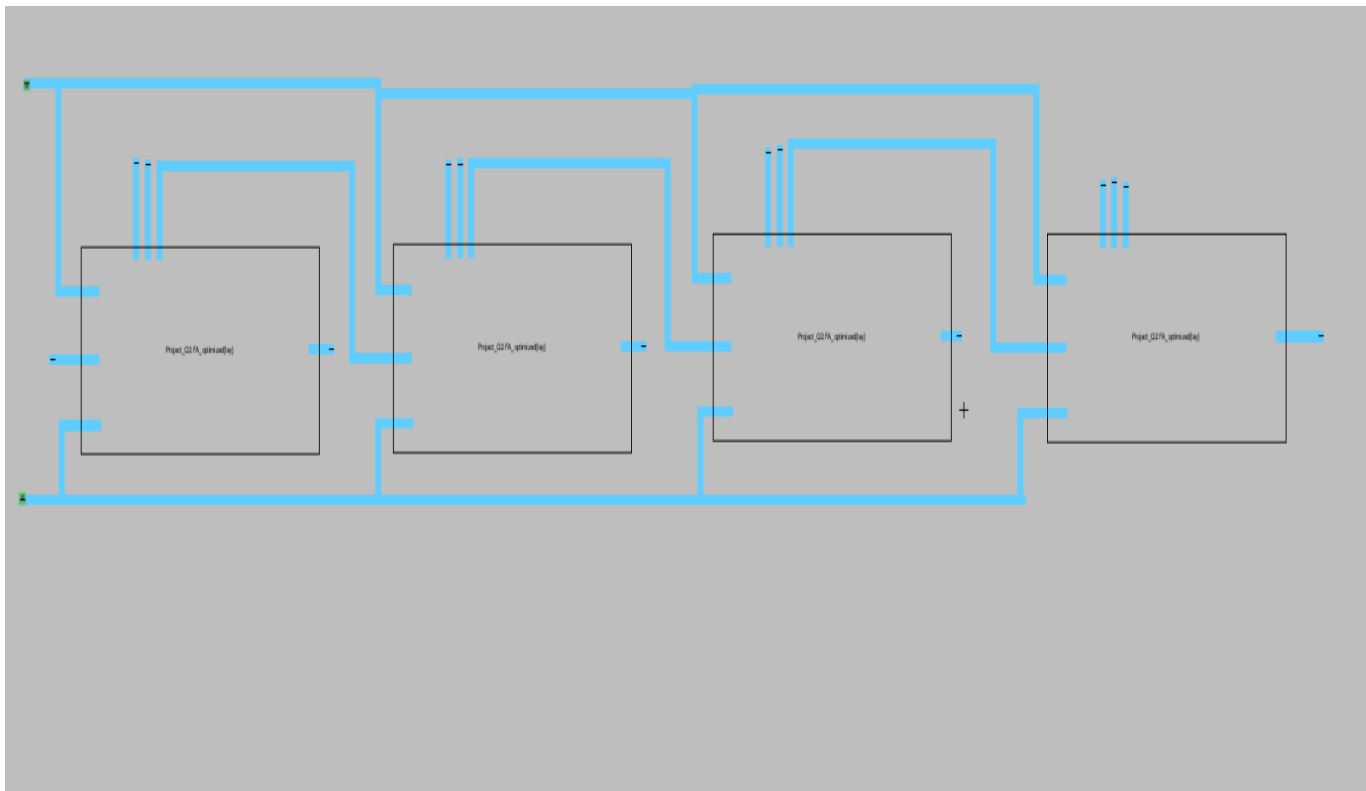
Optimised Four-Bit Adder Layout (by repeating optimised Full Adder Layout Blocks) :




Output Graphs of Optimised Four-Bit Adder using Schematic Simulations :


Case 1 : $a_0, a_1, a_2, a_3 = 1 \rightarrow 0$; $b_0, b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$

 

 



Case 2 : $a_0, a_1, a_2 = 0 \rightarrow 1$; $b_0, a_3 = 1 \rightarrow 0$; $b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 1 \rightarrow 0$

 

 

 Case 3 : $a_0, a_2, b_1 = 0 \rightarrow 1$; $a_1, b_0, a_3, b_3, b_2 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$




 


Critical Path Delays for Optimised Four-Bit Adder :

(We use S3 for critical path delay)

 Case 1 : $a_0, a_1, a_2, a_3 = 1 \rightarrow 0$; $b_0, b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 0 \rightarrow 1$




$tp_{LH} = 647.94 \text{ ps}$

 


$tp_{HL} = 797.66 \text{ ps}$

Propagation delay = $(tp_{LH} + tp_{HL})/2 = 722.8 \text{ ps}$

 Case 2 : $a_0, a_1, a_2 = 0 \rightarrow 1$; $b_0, a_3 = 1 \rightarrow 0$; $b_1, b_2, b_3 = 1 \rightarrow 0$; $C_{in} = 1 \rightarrow 0$




tpHL = 879.95 ps

 


tpLH = 835.30 ps

Propogation delay = (tpLH + tpHL)/2 = 857.62 ps

 Case 3 : a0, a2, b1 = 0 → 1; a1, b0, a3, b3, b2 = 1 → 0; Cin = 0 → 1 :



tpLH = 763.60 ps

 

tpHL = 669.20 ps

Propagation delay = (tpLH + tpHL)/2 = 716.4 ps

Conclusion:

By optimizing the Full Adder design, we achieved a significant reduction in propagation delay. This improvement enhances the overall speed and performance of the 4-bit Adder, making it more efficient for digital circuit applications. The results validate the effectiveness of our optimization approach in high-speed arithmetic unit design.

Teamwork Distribution:

Team Members Name	Contribution
Mehak	Schematic full adder(unoptimised)+propagation delay simulations of unoptimised full adder +full adder layout + 4 bit adder schematic
Jatin	Schematic full adder(optimised)+propagation delay simulations of optimised full adder + full adder layout + 4 bit adder schematic
Harshith	Schematic full adder(optimised)+propagation delay simulations of optimised full adder + full adder layout + 4 bit adder layout and schematic
Ruthwik	Schematic full adder(unoptimised)+propagation delay simulations of unoptimised full adder + full adder layout